

Using the mesh-current method, calculate the power dissipated in each resistor.

$P_{R1} =$  \_\_\_\_\_

$P_{R2} =$  \_\_\_\_\_

$P_{R3} =$  \_\_\_\_\_

$P_{R4} =$  \_\_\_\_\_

