

Using the mesh-current method, calculate the resistor currents, i_{R2} and i_{R5} .

$i_{R2} =$ _____

$i_{R5} =$ _____

