

For the circuit shown below, use the *source transformation* method to find the current i_{R6} . Your procedure will require some “sidesteps” as you work to combine sources and resistors. It is probably a good idea to include sketches of intermediate circuits as you transform your way to a final circuit.

$i_{R6} =$ _____

