

Using the node-voltage method, calculate the power dissipated in each resistor in the circuit.

$P_{R1} =$ _____

$P_{R2} =$ _____

$P_{R3} =$ _____

