

For the circuit below, find the parameters for the Thevenin and Norton equivalent circuits.

$V_{Th} =$ _____

$I_N =$ _____

$R_{Th} =$ _____

