

A switching voltage source is connected directly across a $100\text{-}\mu\text{H}$ inductor. The voltage source is constant at 5 V for $100\text{ }\mu\text{s}$ and is then switched to a constant of -2 V for $250\text{ }\mu\text{s}$. the cycles then repeats.

Make a good *quantitative* sketch of the inductor current as a function of time.

You can assume the the inductor current is 0 at $t = 0$.

How would the sketch change if the voltage source were at -2 V for only 2 ms ? If the voltage source kept switching back and forth forever, what would be the eventual inductor current after a very long time?