

- a) Design a passive first-order high-pass filter using resistors and an inductor. The filter should have a corner frequency at 12 kHz and high frequency gain of 0.33.

- b) Confirm your design with a SPICE frequency response simulation. In the simulation, use a frequency range of 10 Hz to 1 MHz. Plot the magnitude of the output over this range.