

Design a second-order band-pass filter having  $f_o = 5000$  Hz, bandwidth = 2500 Hz, and  $G_o = 0.5$ .

With  $G_o < 1$ , it appears that this should be a passive filter. You can use either a series or parallel arrangement. Use  $L = 15$  mH in your design. Then try to choose resistors and the capacitor with standard values, and meet the specs within  $\pm 5\%$ .

Confirm your design with a SPICE (PSPICE or LTSPICE) frequency response simulation. Then run a second simulation, but include a  $5\text{-}\Omega$  resistor in series with the inductor to simulate the parasitic resistance of the inductor. (In LTSPICE, you can add a parasitic resistance directly to the inductor model itself.) Note the differences caused by the parasitic resistance.