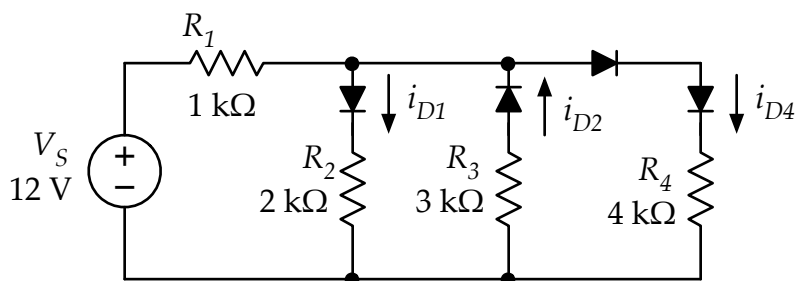


For the diode circuit shown at right, calculate the 3 indicated diode currents.



$i_{D1} =$ _____; $i_{D2} =$ _____; $i_{D4} =$ _____