

For the circuit shown, calculate  $v_{RL}$  for  $V_{BB} = 8$  V. Repeat for  $V_{BB} = 2$  V.

For the *pnp*,  $\beta_F = 50$  and for the *npn*,  $\beta_F = 100$ .

$V_{BB} = 8$  V:  $v_{RL} =$  \_\_\_\_\_

$V_{BB} = 2$  V:  $v_{RL} =$  \_\_\_\_\_

