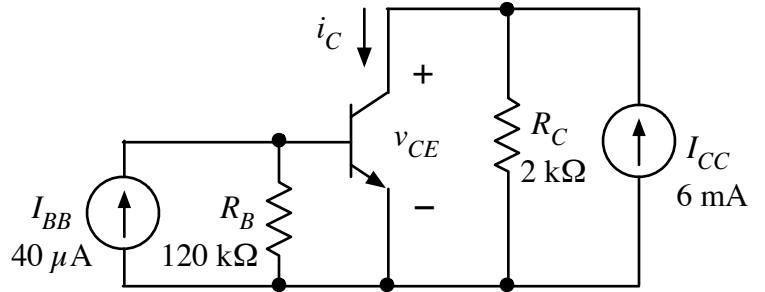


For each of the two NPN transistor circuits shown, calculate i_C and v_{CE} . The NPN BJTs in both circuits have $\beta_F = 100$.

$i_C =$ _____

$v_{CE} =$ _____



$i_C =$ _____

$v_{CE} =$ _____

